

VLSI Course Project

4-Bit CLA adder

Vedant Tejas
2023112018
vedant.tejas@research.iiit.ac.in
UG2, ECD

IIITH

I. INTRODUCTION

4 bit CLA adder adds two 4-bit numbers and gives the final 4-bit sum

However, unlike normal 4-bit Ripple Carry Adder which calculates each carry one at a time, CLA Adder calculates all the carry simultaneously, reducing the propagation delay.

1. Construction and logic:

We have to create three blocks. First we generate **pi** and **gi** (Propagate and Generate) for CLA block

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \cdot b_i$$

Then we calculate all carries in CLA block by following the logic which is given by this equation.

$$c_{i+1} = p_i c_i + g_i$$

From this, we can calculate all carries c_i 's from the propagates and generates (p_i 's and g_i 's).

$$c_1 = (p_0 \cdot c_0) + g_0$$

$$c_2 = (p_1 + p_0 \cdot c_0) + g_1$$

$$c_3 = (p_2 + p_1 + p_0 \cdot c_0) + g_2$$

$$c_4 = (p_3 + p_2 + p_1 + p_0 \cdot c_0) + g_3$$

Finally we can get the final sum by following the logic

$$S_i = p_i \oplus c_i$$

II. DESIGN TOPOLOGY

For XOR, AND & OR gates, we use PTL (Pass Transistor Logic) Topology and CMOS Topology for Inverters.


 
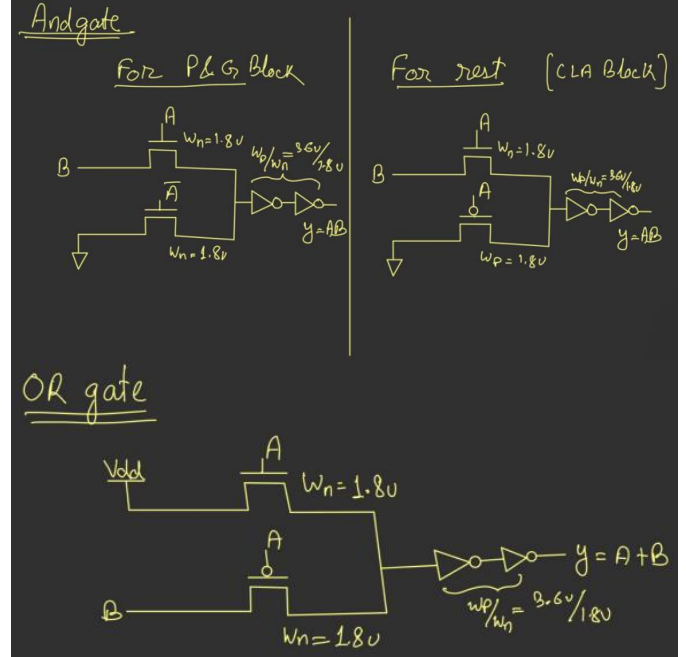
 


Fig. 2: Circuit for CLA Adder

D FLIP FLOP

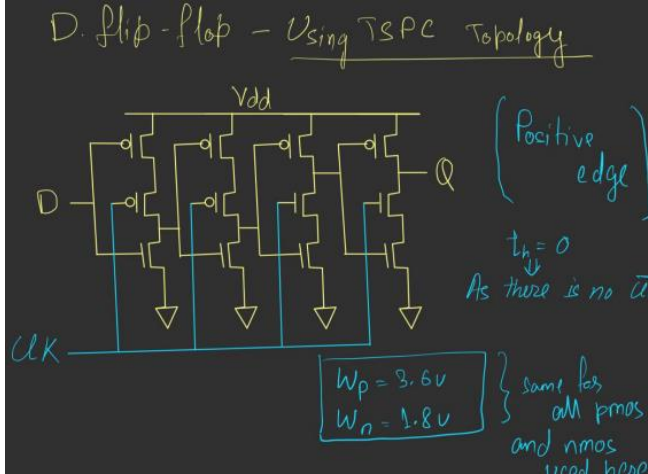For D flipflop, we use TSPC (True Single Phase Clock) topology. Given below is the circuit for flipflop along with its size.



III. PRE-LAYOUT SIMULATIONS IN NGSPICE

CLA ADDER

For CLA Adder, we take input as $a = 1001$ and $b = 1101$ at $t = 5\text{ns}$. The output is as follows.


Here the output is 10110

Thus this cla is working as expected

For the analysis of the propagation delays we are giving $a = 1111$ and $b = 1111$ as well as $\text{cin} = 1$. From here we get output as 11111. Here we see the delays of the sum and final carry unit.

Measurements for Transient Analysis				
tpd_s0	= 4.498190e-11	targ= 5.049982e-09	trig= 5.005000e-09	
tpd_s1	= 4.629391e-10	targ= 5.467939e-09	trig= 5.005000e-09	
tpd_s2	= 8.350323e-10	targ= 5.840032e-09	trig= 5.005000e-09	
tpd_s3	= 8.265227e-10	targ= 5.831523e-09	trig= 5.005000e-09	
tpd_carry	= 7.256877e-10	targ= 5.730688e-09	trig= 5.005000e-09	


 
$\text{Tpd}_{\min} = 44.9\text{ps}$ $\text{Tpd}_{\max} = 83.5\text{ps}$



D-FLIP FLOP

For D-flipflop where assuming a positive edge, we get the following simulation:

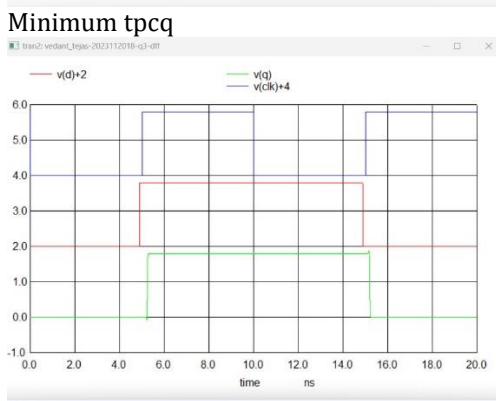 As we can see, Q is updated to D at +ve edge only. Hence its working properly



IV. SETUP TIME, HOLD TIME AND PROPAGATION DELAY FROM CLK TO Q IN FLIPFLOP


We have used TSPC topology for our D-FlipFlop. Since there is no use of (clk)', we have zero hold time ($t_{hold} = 0$). For setup time, we did trial and error and found it to be $t_{setup} = 0.11\text{ns}$. Any input given less than t_{setup} before next +ve edge, either input is not registered or output is being corrupted. For propagation delay from clk to Q (tpcq), we can see the minimum and maximum tpcq. The values are as follows:

Measurements for Transient Analysis				
tpcq_r	=	1.603104e-10	targ=	5.175310e-09 trig= 5.015000e-09
tpcq_f	=	1.133849e-10	targ=	1.512838e-08 trig= 1.501500e-08
tpcq	=	1.36848e-10		

tpcq_r	=	2.335070e-10	targ=	5.248507e-09 trig= 5.015000e-09
tpcq_f	=	1.819591e-10	targ=	1.519696e-08 trig= 1.501500e-08
tpcq	=	2.07733e-10		

$T_{pcqmin} = 0.136\text{ns}$ $T_{pcqmax} = 0.207\text{ns}$

 V STICK DIAGRAMS FOR ALL UNIQUE GATES AND FLIPFLOPS





	PRE-LAYOUT	POST LAYOUT
$T_{PCQ\ MIN}$	0.136NS	0.143NS
$T_{PCQ\ MAX}$	0.207NS	0.288NS

VI POST LAYOUT SIMULATIONS

D-FlipFlop

Here we make the circuit given in MAGIC Layout and perform post-Layout simulations.

  
Here we can see that we get a similar output as pre-layout simulations. However, the tpcq value would be different.



```

tpcq_r      = 1.690268e-10  targ= 5.184027e-09  trig= 5.015000e-09
tpcq_f      = 1.189131e-10  targ= 1.513391e-08  trig= 1.501500e-08
tpcq        = 1.43970e-10

```

 


```

tpcq_r      = 3.889382e-10  targ= 5.403938e-09  trig= 5.015000e-09
tpcq_f      = 1.873369e-10  targ= 1.520234e-08  trig= 1.501500e-08
tpcq        = 2.88138e-10

```

B. CLA-ADDER

 

Here we make the circuit given in MAGIC Layout and perform post-layout simulations. We again perform a simulation with input a = 1001 and b = 1101 at t=5ns and get the following result (next page)

As we can see, with some delay, we get the final output s = 10110 which is the same as pre-layout simulations. By giving a and b as 1111 as well as cin = 1 for s = 1111, we get


Now comparing delays with pre-layout simulations, we get:

```

tpd_s0      = 7.954170e-11  targ= 5.084542e-09  trig= 5.005000e-09
tpd_s1      = 5.824552e-10  targ= 5.587455e-09  trig= 5.005000e-09
tpd_s2      = 6.905608e-10  targ= 5.695561e-09  trig= 5.005000e-09
tpd_s3      = 6.639990e-10  targ= 5.668999e-09  trig= 5.005000e-09
tpd_carry    = 5.585690e-10  targ= 5.563569e-09  trig= 5.005000e-09


```


	PRE-LAYOUT	POST LAYOUT
T _{PCQ MIN}	44.9ps	79.54ps
T _{PCQ MAX}	83.5ps	69ps

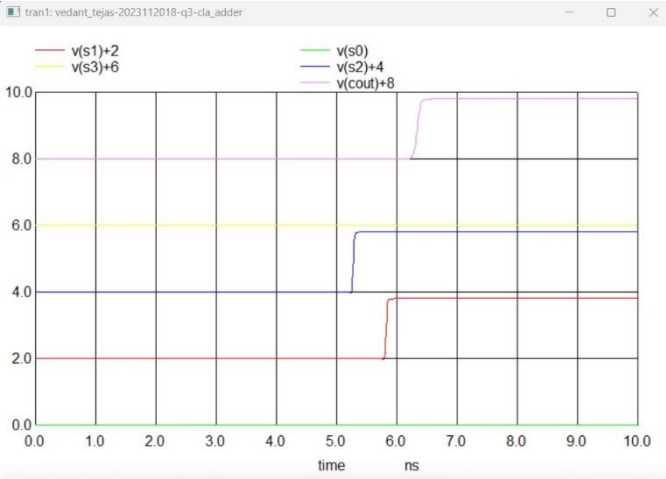

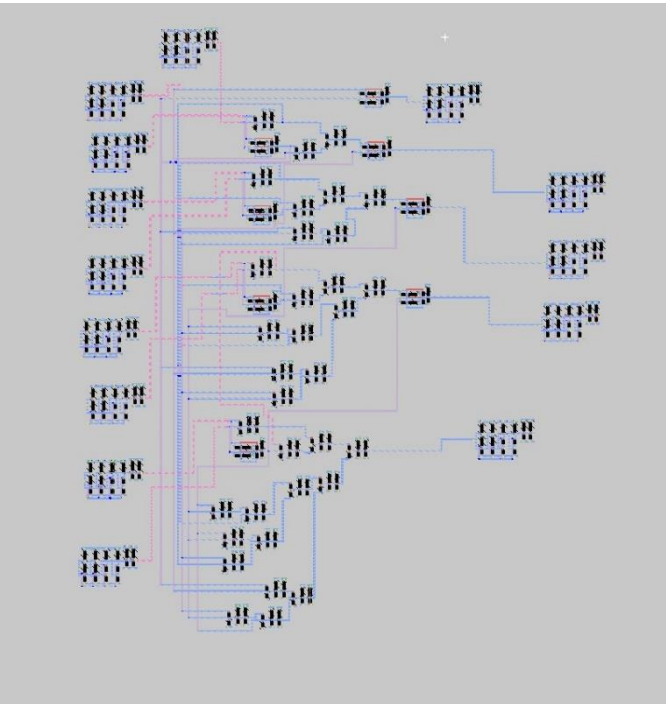VIII. FLOOR PLAN AND MAGIC LAYOUT FOR FINAL CIRCUIT

```
Root cell box:
width x height ( llx, lly ), ( urx, ury ) area (units^2)
microns: 226.08 x 259.56 ( -157.50, -255.51 ), ( 68.58, 4.05 ) 58681.33
lambda: 2512 x 2884 ( -1750, -2839 ), ( 762, 45 ) 7244608
```



X. VERILOG SIMULATIONS AND WAVEFORMS

Now, we create the final CLA Circuit in verilog. We give two inputs, a = 1001, b = 1101 and a = 1010, b = 01101. We get the following output:







```
VCD info: dumpfile tb.vcd opened for output.
a=1001 b=1001      cout=x s=xxxx
a=1100 b=0011      cout=1 s=0010
a=0000 b=0000      cout=0 s=1111
a=0000 b=0000      cout=0 s=0000
[Done] exit with code=0 in 0.119 seconds
```

As we can see, when we give the input, we get the output in the next cycle. We get sum=10110 and sum=01111 after the next input has been given, that is, in the next +ve edge of the clock. In GTKWave, we get the following waveforms:

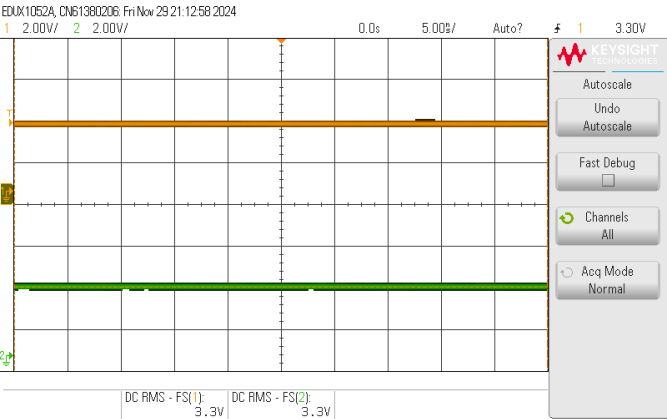  XI. FPGA AND HARDWARE SIMULATIONS

Now, we give inputs in FPGA board and get the output as shown: 1010+0101=1111



 

As we can see, we are getting 3.31V for HIGH (bit 1) and some noise (in mV) for LOW (bit 0). Here we also are getting the sum.

XII. CONCLUSION

So, like this, we are able to design a CLA Adder which takes input at one +ve edge and gives output at next +ve edge clock. This makes sure that the CLA adder has enough time to calculate the sum bits.

REFERENCES

CMOS VLSI design Weste and Harris

Verilog HDL-Samir Palnitkar

Google

IEEE Research Papers